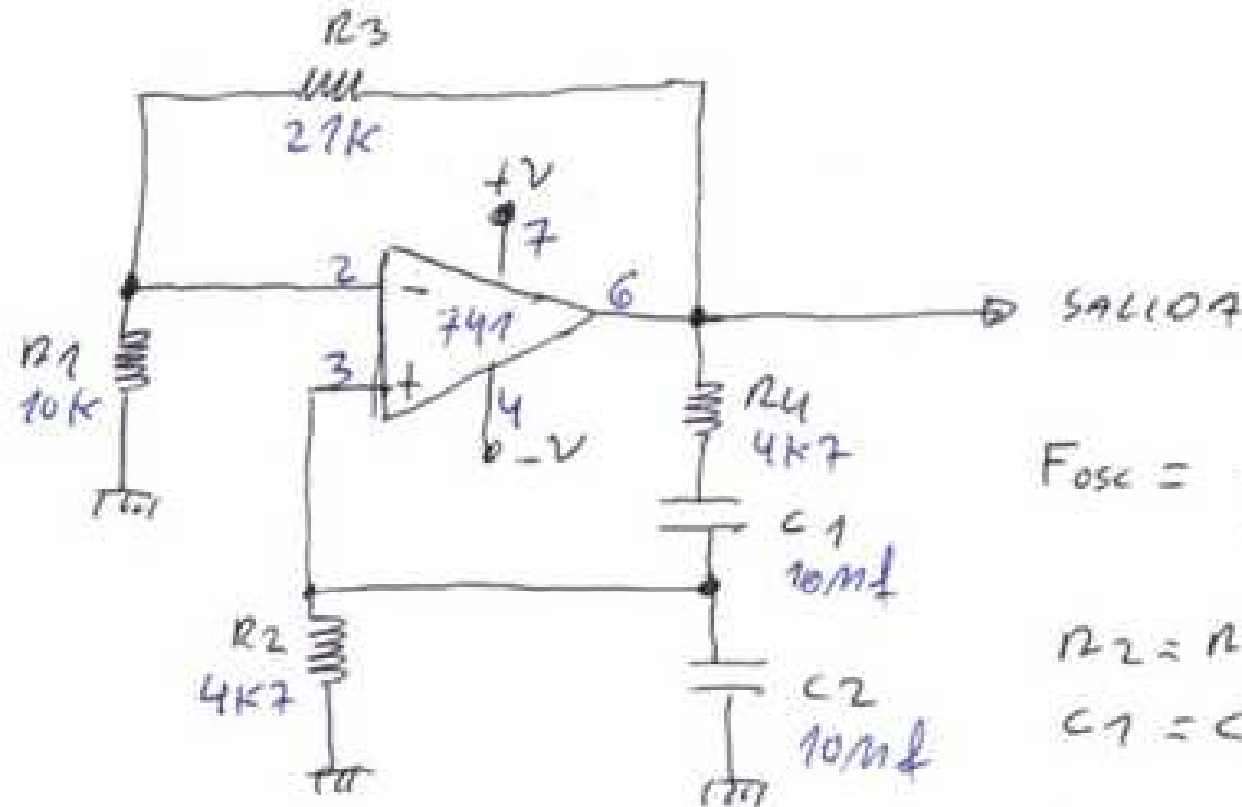


ESQUEMA N:6


OSCILADOR CON OPERACIONAL



$$F_{osc} = \frac{1}{2\pi R_2 C_2}$$

$$R_2 = R_4$$

$$C_1 = C_2$$

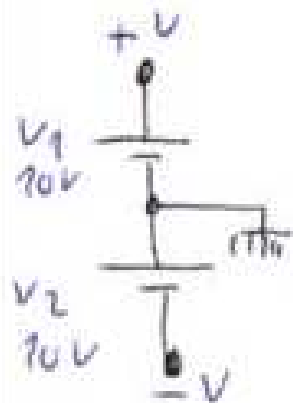

CURSO DE CAD

By Tino Fernández